

Review with Examples

CS207: Digital Logic

Jialin Liu

Department of Computer Science and Engineering (CSE)
Southern University of Science and Technology (SUSTech)

23 December 2022



- ▶ Week 1 (Sept. 9): Lecture 1 - Binary Numbers
- ▶ Week 2 (Sept. 16): Lecture 2 - Boolean Algebra and Logic Gates
- ▶ Week 3 (Sept. 23): Lecture 3 - Gate-Level Minimisation
- ▶ Week 4 (Sept. 30): Lecture 4 - Two/Multi-Level Implementation
- ▶ ——— (Oct. 9): **Assignment 1 Analysis** & Lecture 5 - Combinational Logic
- ▶ Week 5 (Oct. 14): Lecture 6 - Standard Components
- ▶ Week 6 (Oct. 21): Lecture 7 - Arithmetic Circuits
- ▶ Week 7 (Oct. 28): Lecture 8 - Memory Elements: Latches and Flip-flops
- ▶ Week 8 (Nov. 4): Lecture 8 (cont'd) & Lecture 9 - Sequential Logic
- ▶ **Week 9 (Nov. 11): No course (University Sports Day)**



Course Plan

- ▶ **Week 10 (Nov. 18): No course according to University's calendar**
QA Session & Assignment 2 Analysis
- ▶ Week 11 (Nov. 25): Open-book in-class test
- ▶ Week 12 (Dec. 2): Mid-term test Analysis & Assignment 3 Analysis
- ▶ Week 13 (Dec. 9): Lecture 10 - Registers
- ▶ Week 14 (Dec. 16): Lecture 11 - Counters
Project Inspection #1 in lab
- ▶ Week 15 (Dec. 23): Review with Exercise and Solutions
- ▶ **Submission deadline of Assignment 4: 23:55, Dec. 27 (Beijing time)**
- ▶ Week 16 (Dec. 30): Assignment 4 Analysis
Project Inspection #2 in lab
- ▶ **Final exam: 2-4pm, Jan. 4 (Beijing time)**
- ▶ **Online assessment: 2:30-3:30pm, Jan. 4 (Beijing time)**




- ▶ Most digital systems are build with sequential logic.



- ▶ Most digital systems are build with sequential logic.
 - ▶ How to analyse / design **sequential circuits**? (**Lecture 9**)
 - ▶ Commonly used sequential circuits: register (**Lecture 10**) and counter (**Lecture 11**)




- ▶ Most digital systems are build with sequential logic.
 - ▶ How to analyse / design **sequential circuits**? (**Lecture 9**)
 - ▶ Commonly used sequential circuits: register (**Lecture 10**) and counter (**Lecture 11**)
- ▶ A sequential circuit is composed of **feedback path**,
 - ▶ **memory elements** (**Lecture 8**)
 - Different types of memory elements, their characteristic equations/tables.
 - ▶ **combinational circuits**

 



- ▶ Most digital systems are build with sequential logic.
 - ▶ How to analyse / design **sequential circuits**? (**Lecture 9**)
 - ▶ Commonly used sequential circuits: register (**Lecture 10**) and counter (**Lecture 11**)
- ▶ A sequential circuit is composed of **feedback path**,
 - ▶ **memory elements** (**Lecture 8**)
 - Different types of memory elements, their characteristic equations/tables.
 - ▶ **combinational circuits**
 - ▶ How to analyse / design combinational circuits? (**Lecture 5**)
 - Basic notions & logic gates (**Lectures 1 – 2**); Gate-level minimisation (**Lecture 3**); Gate-level implementation (**Lecture 4**)
 - ▶ Standard components: Decoder, encoder, multiplexer, ... (**Lecture 6**)
 - ▶ Arithmetic circuits: adder, subtractor, multiplier, ... (**Lecture 7**)

 

Lectures 8-11
时序逻辑电路
分析与设计
&
记忆模块元件

Lectures 5-7
组合逻辑电路
分析与设计
&
基本模块元件

Lectures 3 & 4
门级电路
化简与实现

Lectures 1 & 2
基础概念和公理

Sequential circuits

- Key difference compared to combinational circuits: memory elements, feedback path
- Representation of sequential circuits: **logic diagram**, function table
- Memory elements: latch & flip-flop (key difference: level sensitive devices vs. edge-sensitive devices)
 - (Controlled) SR latch, (Controlled) D latch, DFF (DFF, diagram, function table), JKFF
- State reduction & state assignment
- **Analysis and design of sequential circuits** (specification -> a logic diagram)

Combinational circuits

- Analysis of combinational circuits: given a diagram, output **Boolean functions** or **truth table**
- **Design of combinational circuits**: specification -> **a logic diagram** / **Boolean functions**
- Standard components: **encoder** (Priority encoder), **decoder** (**minterm generator**), multiplexer (**Boolean function generator**), **magnitude comparator**, **binary adder** (carry, half adder, full adder, carry lookahead logic), **binary subtractor** (borrow, half subtractor, full subtractor, overflow), **binary multiplier** (implementation)

Gate-level design

- Gate-level minimisation: **Boolean Algebra**; **Karnaugh map** (2/3/4-vars K-maps, don't care)
- Implement circuits: **Two/multi-level implementation using NAND, NOR and XOR gates**

- **Number Systems & Conversions**
- **Complement of numbers**
- **Representation of Data -- Code**
(8421BCD, Gray Code)

- **Boolean Algebra & Boolean functions**
- **SOP/POS forms, sum of minterms/maxterms**
- **Logic operators and gates**



Gate-level implementation (Lecture 4)

- ▶ **Two/multi-level implementation** using NAND, NOR and XOR (Lecture 4)
 - based on gate-level minimisation and logic gates
- ▶ **Gate-level minimisation**
 - ▶ **Karnaugh map** (Lecture 3)
 - ▶ 2/3/4-vars K-maps
 - ▶ don't care
 - ▶ **Boolean Algebra** (Lecture 2)
 - ▶ Besides simplifying a Boolean function, expressing a function in sum of minterms / product of maxterms also requires Boolean Algebra.
 - based on basic notions in Lectures 1&2 (number systems, conversions; logic operators and gates)



Recall Boolean Algebra (Lecture 2)

Exercise

Express the function $F(A, B, C, D) = B'D + A'D + BD$ as a sum of minterms with \sum and as a product of maxterms with \prod .



Recall Boolean Algebra (Lecture 2)

Exercise

Express the function $F(A, B, C, D) = B'D + A'D + BD$ as a sum of minterms with Σ and as a product of maxterms with Π .

Solution:

$$\begin{aligned} F(A, B, C, D) &= B'D + A'D + BD \\ &= (A + A')B'(C + C')D + A'(B + B')(C + C')D + (A + A')B(C + C')D \\ &= AB'CD + A'B'CD + AB'C'D + A'B'C'D + \\ &\quad A'BCD + A'B'CD + A'BC'D + A'B'C'D + \\ &\quad ABCD + A'BCD + ABC'D + A'BC'D \\ &= \Sigma(1, 3, 5, 7, 9, 11, 13, 15) \\ &= \Pi(0, 2, 4, 6, 8, 10, 12, 14) \end{aligned}$$



Recall K-map (Lecture 3)

Exercise

Simplify the following Boolean function F together with the don't-care conditions d :

$F(A, B, C, D) = \sum(2, 4, 10, 12, 14, 15)$, $d(A, B, C, D) = \sum(0, 1, 3)$ using **K-map**. Truth table is not necessary.



Recall K-map (Lecture 3)

Exercise

Simplify the following Boolean function F together with the don't-care conditions d :

$F(A, B, C, D) = \sum(2, 4, 10, 12, 14, 15)$, $d(A, B, C, D) = \sum(0, 1, 3)$ using **K-map**. Truth table is not necessary.

Solution:

AB \ CD	00	01	11	10
00	m_0	m_1	m_3	m_2
01	m_4	m_5	m_7	m_6
11	m_{12}	m_{13}	m_{15}	m_{14}
10	m_8	m_9	m_{11}	m_{10}

AB \ CD	00	01	11	10
00	X	X	X	1
01	1			
11	1		1	1
10				1

AB \ CD	00	01	11	10
00	X	X	X	1
01	1			
11	1		1	1
10				1

$$F(A, B, C, D) = BC'D' + ABC + B'CD'$$

Two/multi-level implementation: NAND and NOR Circuits (Lecture 4)



- ▶ NAND gates (与非门) and NOR gates (或非门) are called **universal gates** or **universal building blocks**. Any type of gates or logic functions can be implemented by these gates.
- ▶ Two- and multi-level implementations:
 - ▶ Procedure of two-level implementations using NAND or NOR gates.
 - ▶ Procedure of multi-level implementations using NAND or NOR gates.
- ▶ Exclusive-OR gate for constructing error detection circuits.




Two/multi-level implementation (Lecture 4)


NAND Circuits

- ▶ A convenient way to implement a Boolean function with NAND gates:
 1. Obtain its simplified Algebraic expression.
 2. Convert the Algebraic expression to NAND logic.
- ▶ To facilitate the conversion to NAND logic, it is convenient to define an **alternative** graphic symbol for the gate.

AND-invert:

 

Invert-OR:

 



Two/multi-level implementation (Lecture 4)

NAND Circuits: Procedure

- ▶ A Boolean function can be implemented with **two levels of NAND gates**.
 1. Simplify the Algebraic expression and express it in **sum-of-products form**.
 2. Draw **a NAND gate for each product term** of the expression that has **at least two literals**.
The inputs to each NAND gate are the literals of the term. This procedure produces a group of **first-level gates**.
 3. A term with **a single literal requires an inverter** in the first level. However, if the single literal is complemented, it can be connected directly to an input of the second-level NAND gate.
 4. Draw **a single gate** using the **AND-invert** or the **invert-OR** graphic symbol **in the second level**, with inputs coming from outputs of first-level gates.



C.f. Example of Lecture 4 (pages 25-33)



Two/multi-level implementation (Lecture 4)

Multilevel NAND Circuits

- Convert the following multilevel AND–OR diagram into an all-NAND diagram using mixed notation.
- 1. Convert all AND gates to NAND gates with AND-invert graphic symbols.
- 2. Convert all OR gates to NAND gates with invert-OR graphic symbols.
- 3. Check all the bubbles in the diagram. For every bubble that is not compensated by another small circle along the same line, insert an inverter (a one-input NAND gate) or complement the input literal.

  





NOR Circuits (Lecture 4)

- ▶ To facilitate the conversion to NOR logic, it is convenient to define an alternative graphic symbol for the gate.

OR-invert:

 

Invert-AND:

 

- ▶ **Procedure:**

- ▶ A two-level implementation with NOR gates requires that the function be simplified into **product-of-sums form**.
- ▶ Change the OR gates to NOR gates with OR-invert graphic symbols and the AND gate to a NOR gate with an invert-AND graphic symbol.

- ▶ **Remark:** The equivalent AND-OR diagram can be recognised from the NOR diagram by removing all the bubbles.



Combinational Circuits (Lectures 5 – 7)

- ▶ Combinational circuit consists of logic gates whose outputs at any time are determined from only the present combination of inputs.
 - ▶ **Procedure of analysing combinational circuits** (Lecture 5)
 - ▶ Given a diagram, output Boolean functions or truth table
 - ▶ **Procedure of designing combinational circuits** (Lecture 5)
 - ▶ Specification -> a logic diagram / Boolean functions
 - ▶ **Standard components** (Lecture 6)
 - ▶ Encoder (Priority encoder), decoder (minterm generator), multiplexer (Boolean function generator) → Very important!
 - ▶ magnitude comparator
 - ▶ **Arithmetic circuits** (Lecture 7)
 - ▶ Binary adder (carry, half adder, full adder, carry lookahead logic), binary subtractor (borrow, half subtractor, full subtractor, overflow), binary multiplier (implementation)



Combinational Circuits (Lecture 5)

Procedure of analysing combinational circuits

► **Input:** a logic diagram.

1. **Make sure that the given circuit is combinational and not sequential.**

- The diagram of a combinational circuit has logic gates with **no feedback paths or memory elements**.
- **Feedback path:** a connection from the output of one gate to the input of a second gate whose output forms part of the input to the first gate.

2. **Obtain the output Boolean functions from the given diagram:**

- 2.1 Label all gate outputs that are a function of input variables with arbitrary symbols – but with meaningful names (i.e., only inputs, no other intermediate variables). Determine the Boolean functions for each gate output.
- 2.2 Label the gates that are a function of input variables and previously labeled gates with other arbitrary symbols. Determine their Boolean functions.
- 2.3 Repeat the process outlined in **step 2.2** until the outputs of the circuit are obtained.
- 2.4 By repeated substitution of previously defined functions, obtain the output Boolean functions in terms of input variables.

► **Output:** a set of Boolean functions.



Combinational Circuits (Lecture 5)

Procedure of designing combinational circuits

- ▶ Design of combinational circuits: develop a logic circuit diagram or a set of Boolean functions from specification of the design objective.
 - ▶ Input: a specification of the design objective.
 - ▶ Output: a logic circuit diagram or a set of Boolean functions.
- ▶ Steps:
 - ▶ From the specifications of the circuit, determine the required number of inputs and outputs and assign a symbol to each.
 - ▶ Derive the truth table that defines the required relationship between inputs and outputs.
 - ▶ Obtain the simplified Boolean functions for each output as a function of the input variables.
 - ▶ Draw the logic diagram and verify the correctness of the design (manually or by simulation).

←C.f. Example of Lecture 5 (pages 21-26)



Exercise

Convert from BCD code to excess-3 code (i.e., self-complementary BCD code used to represent the decimal numbers).

Decimal digit	BCD code				Excess-3 code			
	A	B	C	D	w	x	y	z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0



Procedure:

1. From the specifications of the circuit, determine the required number of inputs and outputs and assign a symbol to each.
→ Each code uses 4 bits, therefore 4 input bits and 4 output bits.
2. Derive the truth table that defines the required relationship between inputs and outputs.
→ We already have the truth table :)
3. Obtain the simplified Boolean functions for each output as a function of the input variables.
→ Use K-map!
4. Draw the logic diagram and verify the correctness of the design.

AB \ CD	00	01	11	10
00				
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$$w = A + BD + BC$$

AB \ CD	00	01	11	10
00		1	1	1
01	1			
11	X	X	X	X
10		1	X	X

$$x = BC'D' + B'D + B'C$$



$$y = C'D' + CD$$

AB \ CD	00	01	11	10
00	1		1	
01	1		1	
11	X	X	X	X
10	1		X	X


$$z = D'$$

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1		X	X



► We manipulate these Boolean functions **to reuse common gates**:

 - $w = A + BC + BD = A + B(C + D)$.
- $x = B'C + B'D + BC'D' = B'(C + D) + B(C + D)'$.
- $y = CD + C'D' = CD + (C + D)'$.
- $z = D'$.



$$w = A + B(C + D), \quad x = B'(C + D) + B(C + D)', \quad y = CD + (C + D)', \quad z = D'.$$



Standard Components (Lecture 6)

- ▶ Standard components: combinational circuits that are employed extensively in the design of digital systems.
 - ▶ Decoders
 - ▶ Encoders
 - ▶ Multiplexers
 - ▶ Comparators.
- ▶ Available in integrated circuits as medium-scale integration (MSI) circuits, also used as standard cells in complex very large-scale integrated (VLSI) circuits.



Standard Components (Lecture 6)

Decoder (译码器)

- ▶ A **decoder** is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.
 - ▶ The selected output is identified either by a 1, when all other outputs are 0, or by a 0 when all other outputs are 1.
 - ▶ The basic function of a decoder having n inputs is to select 1-out-of- 2^n output lines.
- ▶ Main applications:
 - ▶ **Minterm generator** (函数最小项发生器): Generate the 2^n (or fewer) minterms of n input variables. → **Example on page 20 of Lecture 6 & Assignment 2**
 - ▶ **Demultiplexer** (数据分配器): A decoder with enable input can function as a **demultiplexer** – a circuit that receives information from a single line and directs it to one of 2^n possible output lines.
 - ▶ **Address decoder** (地址解码器): Identify a memory cell, disk sector, or other memory or storage device, to ensure one device can communicate with the processor at one time.



Standard Components (Lecture 6)

Encoder (编码器)

- ▶ An **encoder** performs the inverse operation to that of a decoder.
- ▶ Example: Octal-to-binary encoder.
 - ▶ Eight inputs and three outputs connected with OR.
 - ▶ Only one input can be active for one time.

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1


→ Example on pages 27 – 30 of Lecture 6 & Assignment 2



Standard Components (Lecture 6)

Multiplexer (数据选择器/多路复用器)

- ▶ A **multiplexer (MUX)** (数据选择器/多路复用器) is a combinational circuit that selects binary information **from one of many input lines** and directs it to a single output line.
- ▶ It selects 1-out-of- n lines where n is usually 2, 4, 8, or 16.
- ▶ Example: 4-to-1 MUX
 - ▶ A block diagram of a multiplexer having 4 input data lines d_0 , d_1 , d_2 , and d_3 and complementary outputs f and f' .
 - ▶ its characteristic equation is $f = A'B'd_0 + A'Bd_1 + AB'd_2 + ABd_3$.

 

- ▶ Multiplexer as a boolean function generator

→ **Example on pages 36 – 37 of Lecture 6 & Assignment 2**



Exercise


Implement the following Boolean function using a 3-to-8-line decoder: $f(x, y, z) = x'y'z + xy' + yz'$.

Exercise

Implement the following Boolean function using a 3-to-8-line decoder: $f(x, y, z) = x'y'z + xy' + yz'$.

Solution:
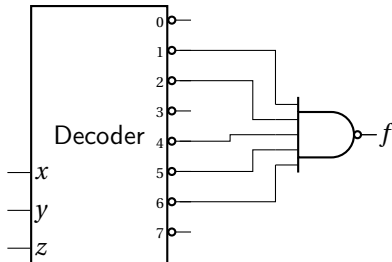
$$\begin{aligned} f(x, y, z) &= x'y'z + xy' + yz' \\ &= x'y'z + xy'z + xy'z' + xyz' + x'yz' \\ &= \sum(1, 5, 4, 6, 2) \end{aligned}$$





Exercise

Implement the following Boolean function using a 4-1 multiplexer: $f(x,y,z) = x'y'z + xy' + yz'$. Let x and y be the control signals.


Exercise

Implement the following Boolean function using a 4-1 multiplexer: $f(x, y, z) = x'y'z + xy' + yz'$. Let x and y be the control signals.



Solution:

$$f(x, y, z) = x'y'z + xy' + yz' = x'y'z + xy' \cdot 1 + xyz' + x'yz'$$

Decimal	x	y	f
0	0	0	z
1	0	1	z'
2	1	0	1
3	1	1	z'

 

$$f(x, y, z) = x'y'z + xy' + yz'$$

  

Encoders and multiplexers can be used to implement any combinatorial circuits.



Arithmetic Circuits (Lecture 7)


- ▶ Standard components: combinational circuits that are employed extensively in the design of digital systems.
 - ▶ Comparators, decoders, encoders, multiplexers, **adders, subtractors and multipliers.**
- ▶ **Adders can be used to implement subtractors and multipliers.**
 - ▶ The subtraction $X - Y$ can be done by taking the 2's complement of Y and adding it to A . Thus, $X - Y = X + 2's \text{ complement of } Y$ (Subtraction \rightarrow Addition)
 - ▶ The 2's complement can be obtained by taking the 1's complement and adding 1 to the least significant pair of bits.
 - ▶ The 1's complement can be implemented with inverters, and a 1 can be added to the sum through the input carry.

$$\begin{array}{r}
 \begin{array}{cc} B_1 & B_0 \\ A_1 & A_0 \\ \hline A_0 B_1 & A_0 B_0 \end{array} \\
 \begin{array}{cc} A_1 B_1 & A_1 B_0 \\ \hline C_3 & C_2 & C_1 & C_0 \end{array}
 \end{array}$$

Half Adder (Lecture 7)

- ▶ A combinational circuit that performs the addition of two bits is called a **half adder**.
- ▶ Design of half adder:
 - ▶ The circuit needs two binary inputs and two binary outputs.
 - ▶ Input variables: the augend (被加数) bit A and addend (加数) bit B .
 - ▶ Output variables: the sum S and carry C .
 - ▶ The simplified SOP expressions can be obtained directly from the **truth table**: $S = A \oplus B$ and $C = AB$.
 - ▶ Logic diagram can be implemented in SOPs.


Input		Output	
A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Full Adder (Lecture 7)


- ▶ Addition of n -bit binary numbers requires the use of a full adder.
- ▶ A **full adder** is a combinational circuit that forms the arithmetic sum of three bits
 - ▶ Input variables:
 - ▶ A and B : the two significant bits to be added;
 - ▶ X : the carry from the previous lower significant position.
 - ▶ Output variables: sum S and carry C .

Input			Output	
A	B	X	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Binary Adder (Lecture 7)

- ▶ A **binary adder** is a digital circuit that produces the arithmetic sum of two binary numbers.
- ▶ It can be constructed with full adders connected in cascade, i.e., **ripple-carry-adder** (串行进位加法器), with the output carry from each full adder connected to the input carry of the next full adder in the chain.
- ▶ Addition of n -bit numbers requires a chain of n full adders or a chain of 1 half adder and $n - 1$ full adders.

 

The 4-bit adder is a typical example of a standard component.



Exercise

Design a binary multiplier that multiplies a 4-bit number, $B_3B_2B_1B_0$, by a 3-bit number $A_2A_1A_0$. The circuit is to be implemented using AND gates and full adders.



Exercise

Design a binary multiplier that multiplies a 4-bit number, $B_3B_2B_1B_0$, by a 3-bit number $A_2A_1A_0$. The circuit is to be implemented using AND gates and full adders.

Solution:

“For J multiplier bits and K multiplicand bits, we need $J \times K$ AND gates and $J - 1$ K -bit adders to produce a product of $(J + K)$ bits.” [1]

- ▶ There are 3 multiplier bits and 4 multiplicand bits, hence $K = 4$ and $J = 3$.
- ▶ Twelve AND gates and two 4-bit adders are needed to produce a product of 7 bits.

[1] M. M. Mano and M. Ciletti, *Digital design: with an introduction to the Verilog HDL*. Pearson, 2013

“For J multiplier bits and K multiplicand bits, we need $J \times K$ AND gates and $J - 1$ K -bit adders to produce a product of $(J + K)$ bits.” [1]

- ▶ There are 3 multiplier bits and 4 multiplicand bits, hence $K = 4$ and $J = 3$.
- ▶ Twelve AND gates and two 4-bit adders are needed to produce a product of 7 bits.

[1] M. M. Mano and M. Ciletti, *Digital design: with an introduction to the Verilog HDL*. Pearson, 2013

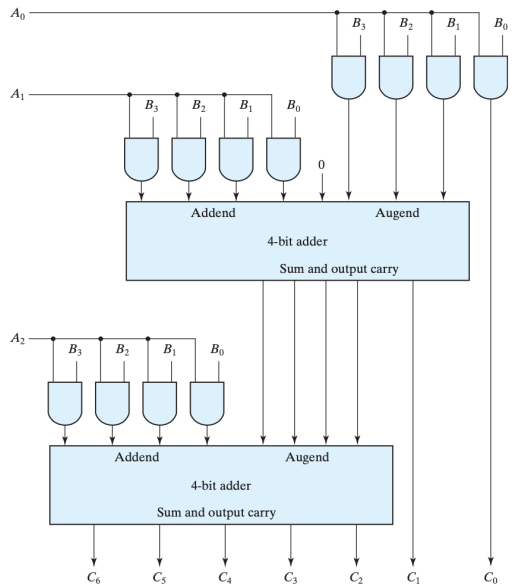


FIGURE 4.16
Four-bit by three-bit binary multiplier



Sequential Circuits (Lectures 8 – 11)

- ▶ Sequential circuit: specified by a time sequence of inputs, outputs, and internal states.
- ▶ A **combinational circuit**, but with **memory elements** (记忆元件) connected in a **feedback path** (反馈回路).
 - ▶ **Memory elements**: SR latch, Controlled SR latch, Controlled D latch, DFF, JKFF, TFF (Lecture 8)
 - ▶ **Procedure of analysing sequential circuits** (Lecture 9)
 - ▶ Diagram -> a table for the time sequence of inputs, outputs, and internal states. Or obtain the Boolean expressions that describes the behaviour of the circuit.
 - ▶ **Procedure of designing sequential circuits** (Lecture 9)
 - ▶ Specification -> a state table and logic diagram.
 - ▶ **Register** (Lecture 10)
 - ▶ **Counter** (Lecture 11)



Vocabulary

- ▶ Synchronous Sequential Circuits (同步时序电路).
- ▶ Asynchronous sequential circuit (异步时序电路).
- ▶ clock pulse (时钟脉冲), denoted by `clock` or `clk`.
- ▶ Level sensitive device. (时钟信号电平敏感的存储单元电路).
- ▶ Edge-sensitive devices (时钟信号边沿敏感的存储单元电路).
- ▶ Memory elements (记忆元件):
 - ▶ Flip-flop (触发器) (FF).
 - ▶ Latch (锁存器).
- ▶ Set: S (置位), usually means “set the state set to 1”.
- ▶ Reset: R (复位), usually means “set the state to 0”.
- ▶ Present state: Q_t or Q (现态).
- ▶ Next State: Q_{t+1} or Q' (次态).
- ▶ Ways to describe a sequential circuit:
K-map (卡诺图), logic diagram (逻辑电路图), function table (功能表), state table (状态表), state diagram (状态图), characteristic equations (特性方程) (next state equation, 次态方程), excitation table (激励方程).



Characteristic Tables & Characteristic Equations

- ▶ A **characteristic table** describes the logical properties of a flip-flop by describing its operation in tabular form.
- ▶ A **characteristic equation** describes the logical properties of a flip-flop by describing its Boolean function.
- ▶ DFF: $Q_{t+1} = D$.
- ▶ JKFF: $Q_{t+1} = JQ'_t + K'Q_t$.
- ▶ TFF: $Q_{t+1} = T \oplus Q_t$.

J	K	Q_{t+1}	
0	0	Q_t	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'_t	Complement


D	Q_{t+1}	
0	0	Reset
1	1	Set

T	Q_{t+1}	
0	Q_t	No change
1	Q'_t	Complement

State Equations or Transition Equations

- ▶ The behaviour of a sequential circuit can be described with **state equations**, or **transition equations**.

 
- ▶ Two D flip-flops: according to $Q_{t+1} = D$,
 - ▶ $A_{t+1} = A_t x_t + B_t x_t$,
 - ▶ $B_{t+1} = A'_t x_t$.
- ▶ The output:
 - ▶ $y_t = [A_t + B_t] x'_t$.
 - ▶ Since all signals are labeled by t , we can also write $y = (A + B)x'$.





State Diagrams & State Tables

 - ▶ Time-sequence of inputs, outputs, FFs of a sequential circuit can be enumerated in a **state table**.
- ▶ **State diagram**:
 - ▶ Each state as a circle.
 - ▶ Transitions between states are directed lines connecting the circles.



Present		Next				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0



Excitation Tables

Q_t	Q_{t+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Q_t	Q_{t+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Present		Input	Next		Flip-flop Inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1



Analysis of Sequential Circuits (Lecture 9)

- ▶ Circuit diagram \rightarrow Equations \rightarrow State table \rightarrow State diagram.
 - ▶ State table is easier to derived from circuit diagram and state equations.
 - ▶ State diagram gives a pictorial view of state transitions.
- ▶ Procedure:
 - ▶ Equations: Express algebraically the logic diagram of the circuit with FF input equations and output equation(s).
 - ▶ State table:
 - ▶ Determining input equations.
 - ▶ Listing binary values for each input equation.
 - ▶ Using the corresponding flip-flop characteristic table to determine next state values.
 - ▶ State diagram: Easy with state table!

\rightarrow Example on pages 16 – 21 of Lecture 9.



Design of Sequential Circuits (Lecture 9)

- ▶ Given a set of specifications:
 - ▶ Different from combinational circuits, a sequential circuit requires a state table.
 - ▶ It consists of choosing the flip-flops and combinational gates.
 - ▶ Number of flip-flops determined from the number of states.
 - ▶ Combinational circuits derived from state table.
 - ▶ Procedure for designing synchronous sequential circuits:
 1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
 2. **Reduce the number of states if necessary. (Example on pages 26 – 33 of Lecture 9)**
 3. Assign binary values to the states.
 4. Obtain the binary-coded state table.
 5. Choose the type of flip-flops to be used.
 6. Derive the simplified flip-flop input equations and output equations.
 7. Draw the logic diagram.
- **Example on pages 40 – 44 of Lecture 9.**



Recap: Question 2 in Assignment 3

Exercise

A sequential circuit has two JK flip-flops A and B and one input x . The circuit is described by the following flip-flop input equations: $J_A = x'$, $K_A = B$, $J_B = x$, $K_B = A'$.

1. Derive the state equations A_{t+1} and B_{t+1} by substituting the input equations for the J and K variables.
2. Draw the state diagram of the circuit.


Solution:

1. According to the characteristic equation of JK FF $Q_{t+1} = JQ'_t + K'Q_t$:

$$A_{t+1} = J_AA' + K'_A A = x'A' + B'A$$

$$B_{t+1} = J_BB' + K'_B B = xB' + AB$$

2. State diagram of the circuit:

 

Present		Input x	Next	
A	B		A	B
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

Commonly Used Circuits That Include Flip-flops (Lectures 10 & 11)



▶ Register:

- ▶ A group of flip-flops, each one of which
 - ▶ shares a common clock and
 - ▶ is capable of storing one bit of binary information.
- ▶ A flip-flop stores one bit of binary information.
 - An n -bit register consists of a group of n flip-flops capable of storing n bits of binary information.
- ▶ In addition to the flip-flops, a register may have combinational gates that perform certain data-processing tasks.

▶ Counter:

- ▶ A special type of register that goes through a predetermined sequence of binary states.



Shift Register (Lectures 10 & 11)

- ▶ A register capable of shifting its binary contents either to the left or to the right is called a **shift register** (移位寄存器). → A chain of FFs in cascade (串联).
- ▶ The shift register permits the stored data to move from a particular location to some other location within the register.
 - ▶ Serial-in serial-out shift register (串入串出移位寄存器).
 - ▶ Serial-in parallel-out shift register (串入并出移位寄存器).
 - ▶ Parallel-in serial-out shift register (并入串出移位寄存器).
 - ▶ Parallel-in parallel-out shift register (并入并出移位寄存器).
- ▶ The shift registers can be used to
 - ▶ transform between parallel/sequential or sequential/parallel data loading/output;
 - ▶ perform arithmetic operations;
 - ▶ perform some other data processing operations.

Representative Applications of Shift Register (Lectures 10 & 11)



- ▶ Sequence generator (序列信号发生器)
- ▶ Serial addition
- ▶ Frequency divider
- ▶ Counters
 - ▶ **ring counter** (环形计数器)
 - ▶ **switch-tail ring counter** or **Johnson counter**
 - ▶ MOD- N counter
 - ▶ (Synchronous / Asynchronous) down counter, up counter, multimode counter

→ **All the examples of Lecture 10 and Lecture 11 are important!**



Exercise

Design a one-input, one-output serial 2's complementer. The circuit accepts a string of bits from the input, and outputs 0's until the first 1 is received. After that, the 2's complement of the input is generated at the output. The circuit can be reset asynchronously to reset the operation.




Solution:

- ▶ The output is 0 for all 0 inputs until the first 1 occurs at which time, the output is 1. Thereafter, the output is the complement of the input. The state diagram has 2 states:
 - ▶ State 0 : Output = Input
 - ▶ State 1 : Output = Complement of input
- ▶ Note an asynchronous **RESET** is needed to reset the operation.
- ▶ Determine the state table and state diagram.

Present state	Input	Next state	Output
A_t	x	A_{t+1}	y
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

or

Present state A_t	Next state A_{t+1}		Output y	
	$x=0$	$x=1$	$x=0$	$x=1$
0	0	1	0	1
1	1	1	1	0

 


- Determine the excitation equation of y and A_{t+1} :

$$y = A'_t x + A_t x' = A_t \oplus x$$

$$A_{t+1} = A'_t x + A_t x' + A_t x = A_t + x$$

But, if $RESET = 1$, $y = 0$ and $A_{t+1} = 0$.

- A DFF can be used to implement the circuit.

 

Lectures 8-11
时序逻辑电路
分析与设计
&
记忆模块元件

Lectures 5-7
组合逻辑电路
分析与设计
&
基本模块元件

Lectures 3 & 4
门级电路
化简与实现

Lectures 1 & 2
基础概念和公理

Sequential circuits

- Key difference compared to combinational circuits: memory elements, feedback path
- Representation of sequential circuits: **logic diagram**, function table
- Memory elements: latch & flip-flop (key difference: level sensitive devices vs. edge-sensitive devices)
 - (Controlled) SR latch, (Controlled) D latch, DFF (DFF, diagram, function table), JKFF
- State reduction & state assignment
- **Analysis and design of sequential circuits** (specification -> a logic diagram)

Combinational circuits

- Analysis of combinational circuits: given a diagram, output **Boolean functions** or **truth table**
- **Design of combinational circuits**: specification -> **a logic diagram** / **Boolean functions**
- Standard components: **encoder** (Priority encoder), **decoder** (**minterm generator**), multiplexer (**Boolean function generator**), **magnitude comparator**, **binary adder** (carry, half adder, full adder, carry lookahead logic), **binary subtractor** (borrow, half subtractor, full subtractor, overflow), **binary multiplier** (implementation)

Gate-level design

- Gate-level minimisation: **Boolean Algebra**; **Karnaugh map** (2/3/4-vars K-maps, don't care)
- Implement circuits: **Two/multi-level implementation using NAND, NOR and XOR gates**

- **Number Systems & Conversions**
- **Complement of numbers**
- **Representation of Data -- Code**
(8421BCD, Gray Code)

- **Boolean Algebra & Boolean functions**
- **SOP/POS forms, sum of minterms/maxterms**
- **Logic operators and gates**